

# Lab Report 5: Design & Simulation of 4-bit adder

ECEN 454/714


3/3/2024

TA: Saichand Samudrala


Ryan Peng

631003156

### Schematic of the 4-bit adder:

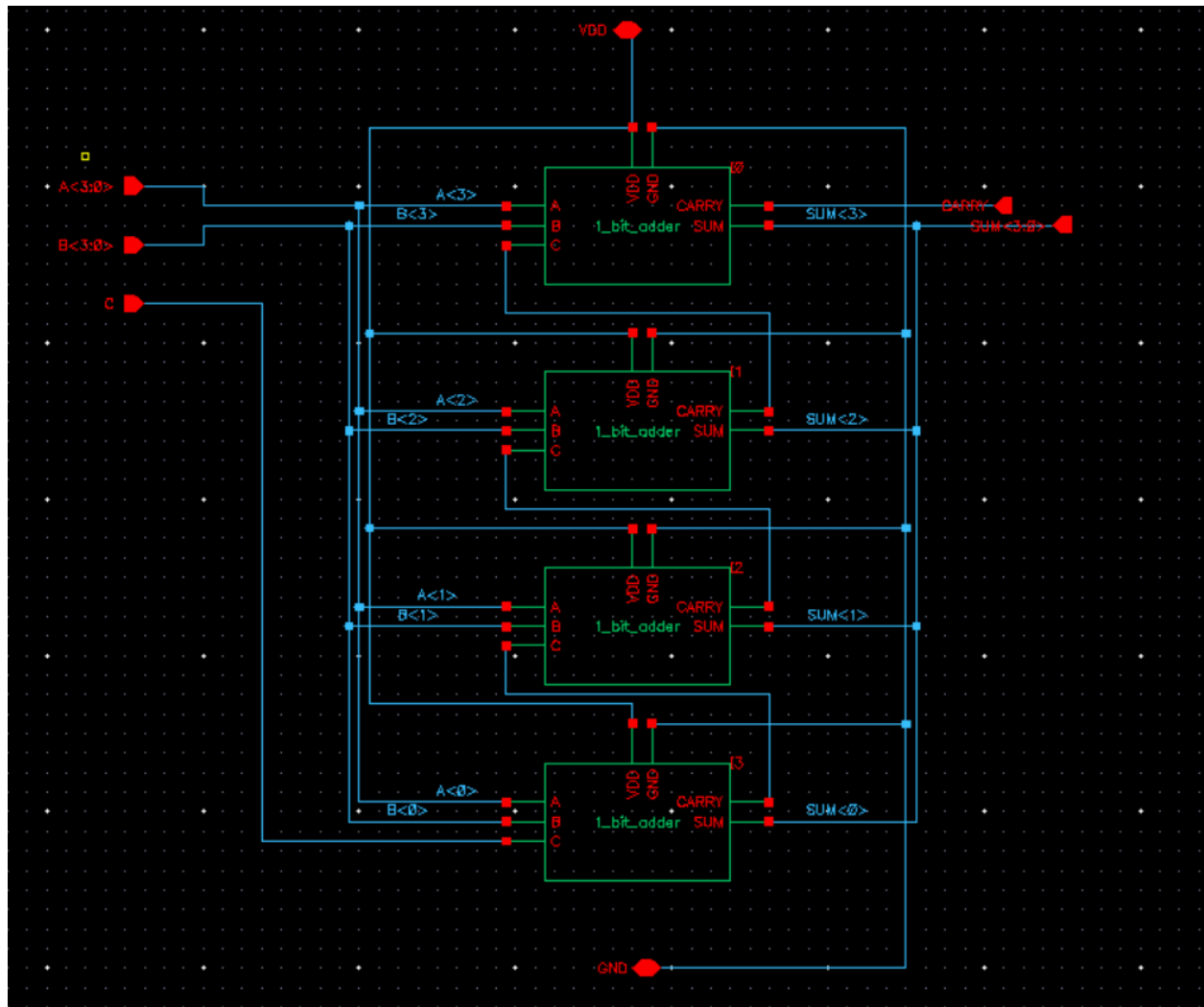

### Layout of the 4-bit adder

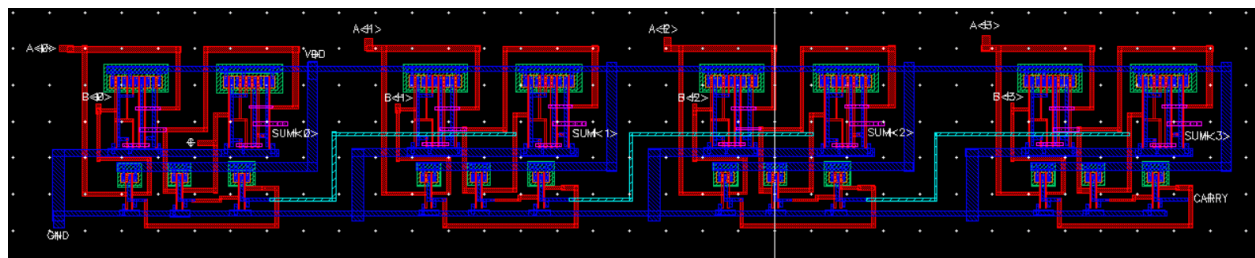

## LVS Results:

```
/home/ugrads/p/pengryan188/ecen714/LVS/si.out@n05-prometheus.olympus.ece.tamu.edu
File Edit View Help cadence

Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/ugrads/p/pengryan188/ecen714/LVS/layout/netlist
count
91      nets
16      terminals
72      pmos
72      nmos

Net-list summary for /home/ugrads/p/pengryan188/ecen714/LVS/schematic/netlist
count
91      nets
16      terminals
72      pmos
72      nmos



Terminal correspondence points
N82      N5      A<0>
N79      N4      A<1>
N76      N3      A<2>
N75      N2      A<3>
N90      N9      B<0>
N87      N8      B<1>
N86      N7      B<2>
N85      N6      B<3>
N81      N10     C
N89      N15     CARRY
N78      N1      GND
N84      N14     SUM<0>
N83      N13     SUM<1>
N80      N12     SUM<2>
N77      N11     SUM<3>
N88      N0      VDD

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.
```

**For: A=0000, B=1111, Carry In=1**

Waveforms:

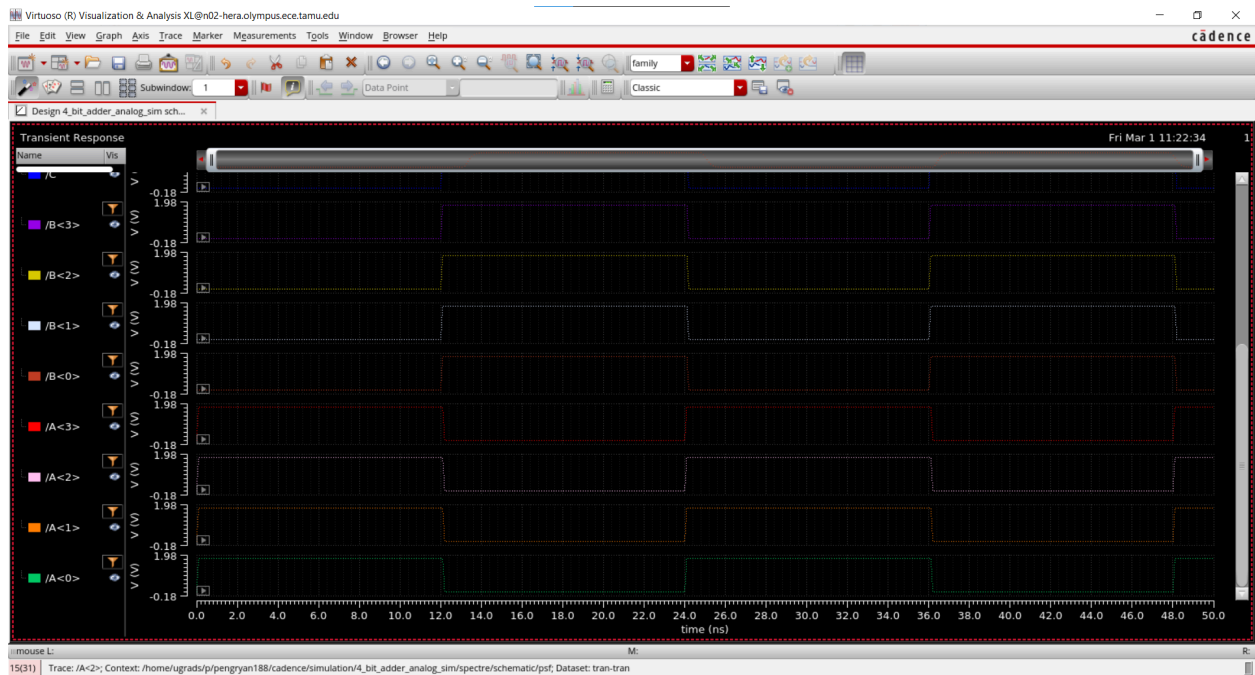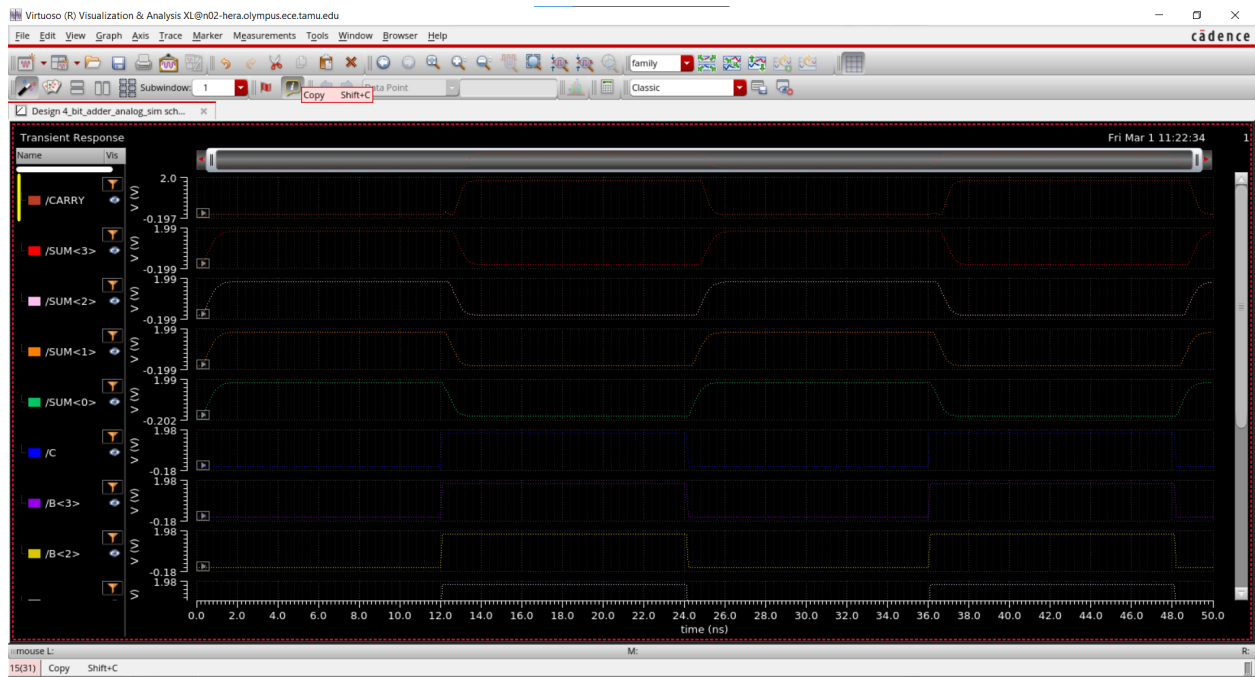

Delay Estimate:

	Rising Delay	Falling Delay	Error %
CARRY	1.0075	1.00056	0.68883
SUM<3>	1.0059	1	0.059
SUM<2>	0.80775	0.8013	0.79851
SUM<1>	0.61394	0.6101	0.62547
SUM<0>	0.42417	0.4221	0.48801

Power:

Expression	Value
1 average(i1("/V0/P...))	-54.46E-6

\* 1.8V = -98.028E-5


**For A=1010 B=0101 Cin = 0:**

Waveforms:






## Delay Estimate:

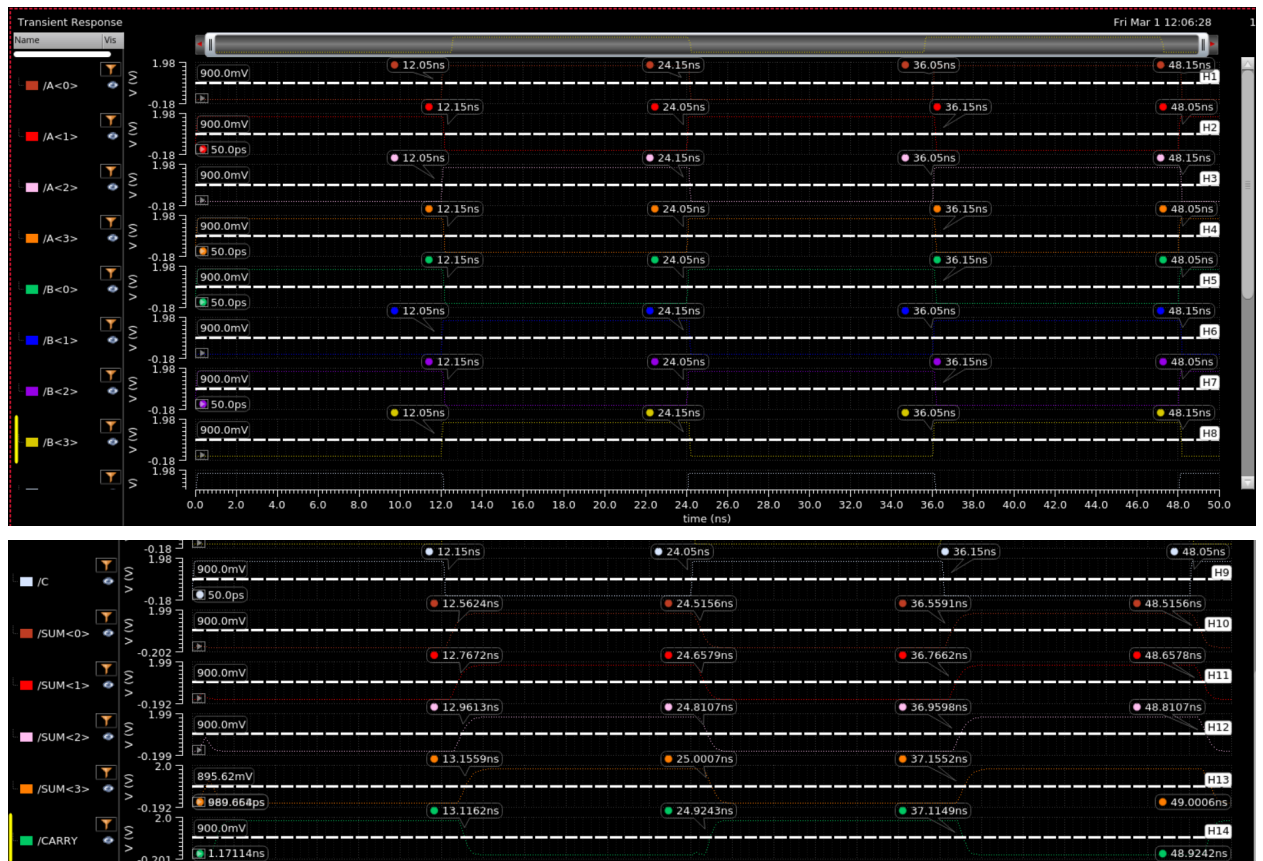



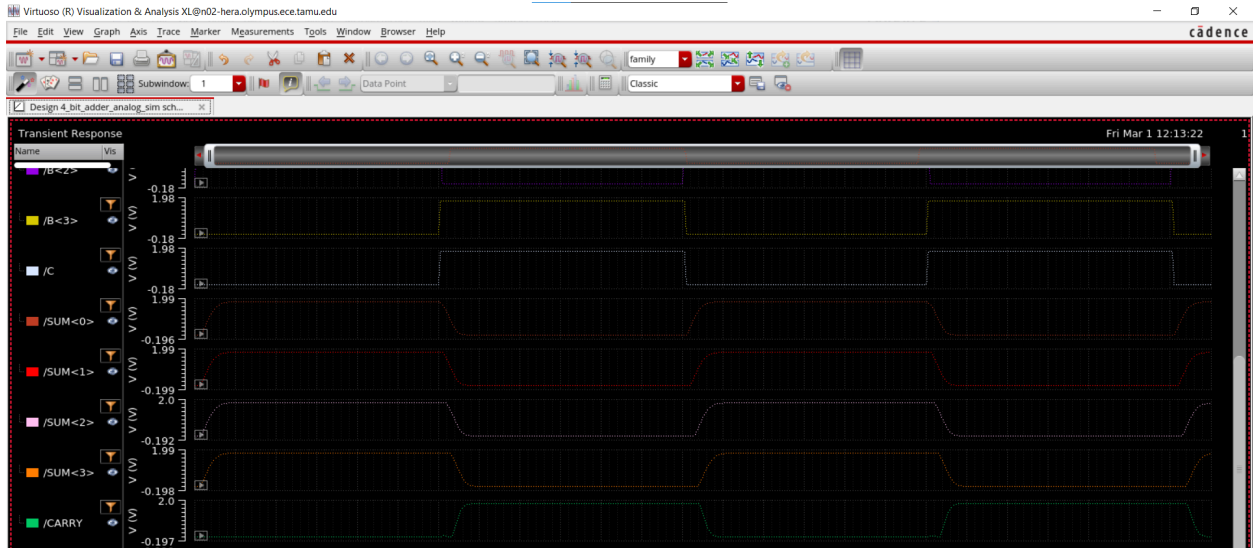

Delay Table:

	Rising Delay	Falling Delay	Error %
CARRY	0.9634	0.8687	10.9
SUM<3>	1.0045	0.9387	7.01
SUM<2>	0.7536	0.8097	7.444
SUM<1>	0.5803	0.6105	5.204
SUM<0>	0.5056	0.5187	2.591



Power:

Expression	Value
1 average(i("/V0/P...))	-54.43E-6

$$* 1.8V = -97.974E-5$$



**A=1100, B=1000, Carry In=0**

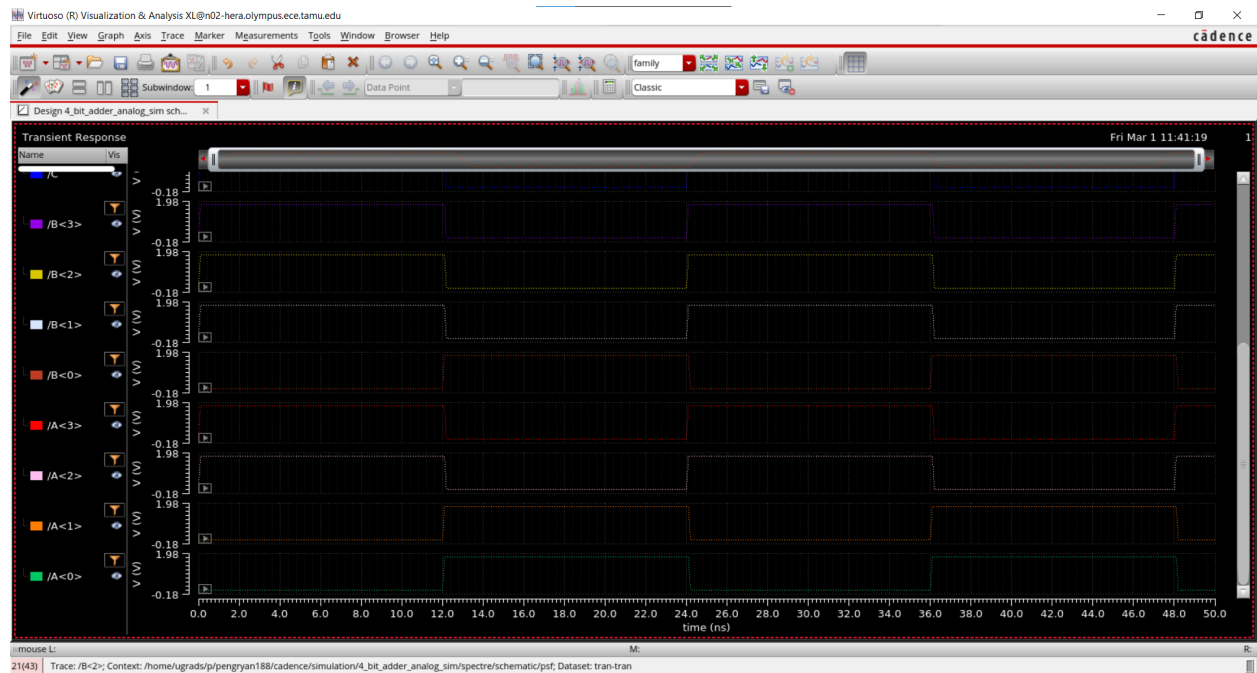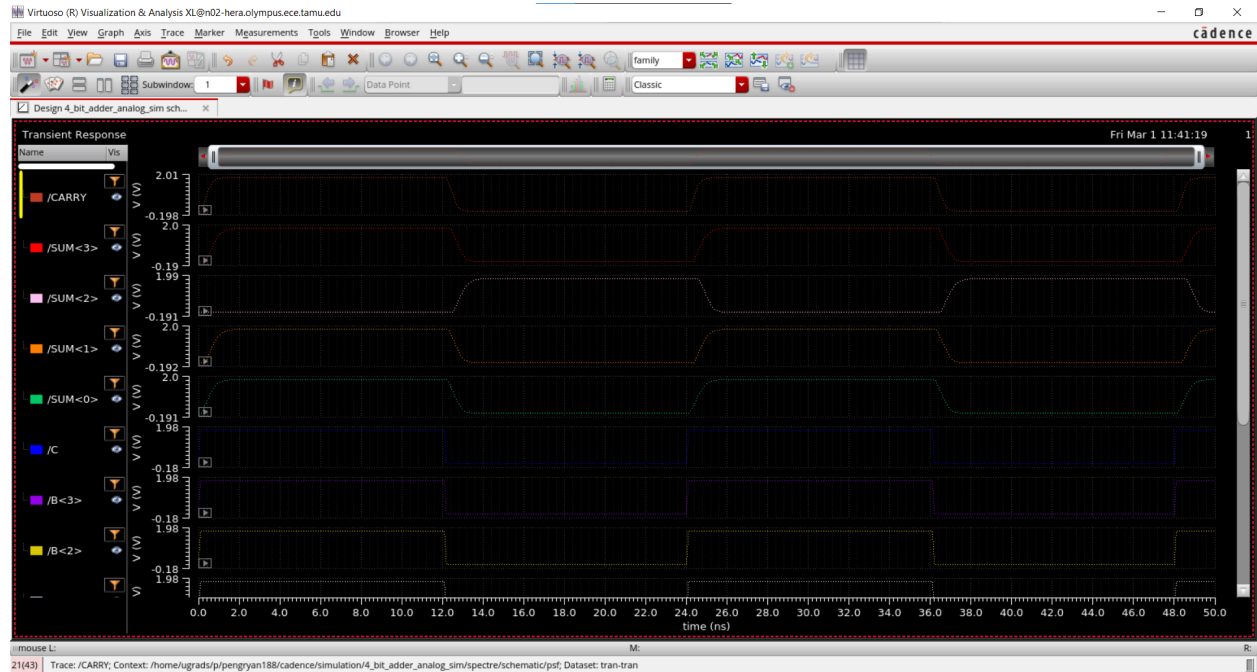

Delay:

	Rising Delay	Falling Delay	Error %
CARRY	0.3597	0.3615	0.5004
SUM<3>	0.635	0.6606	4.031
SUM<2>	0.8502	0.8328	2.089
SUM<1>	0.6297	0.5918	6.404
SUM<0>	0.5716	0.51	12.078

Power:

E average(i("/V0/PLUS" ?result "tran"))	
Expression	Value
1 average(i("/V0/P...	-48.53E-6

x 1.8 = -8.6354E-5